

## **Roll - 200050006**

### **Ques - 3:**

In this question, the task is to design a 4-bit ripple carry adder-subtractor.

'a' and 'b' are the two 4-bit unsigned numbers that are to be added.

'cin' is not an input carry like in the previous question but it is a mode selection bit.

If cin=0 then 'a' and 'b' should be added (a+b).

If cin=1 then 'b' should be subtracted from 'a' (a-b).

'sum' is the 4-bit unsigned addition or subtraction output and

'cout' is the single-bit output carry.

In general, there are 2 ways to subtract a and b. One is the normal borrow method which cannot be used here because we have to use a 4 bit ripple carry adder for subtraction also. The 2nd method is to first take 2's complement of b that is inverse all the bits of b and add 1 to get 2's complement of b and then add a and the 2's complement of b which will finally result in a-b.

### **Method for finding 2's complement of b:**

First we can inverse the bits of b by performing a XOR operation of each of the bits of b with cin=1. This is known as the 1's complement of b. Now to convert 1's complement of b to 2's complement of b, we need to add 1. So instead of adding 1 here, I will give the 4 bit adder a carry of 1 to satisfy the 2's complement of b.

So finally  **$a - b = a + (2's \text{ complement of } b)$**

$$= a + (1's \text{ complement of } b + 1)$$

$$= a + (1's \text{ complement of } b) + (\text{carry} = 1)$$


### **When cin = 0**

Input will be 'a', 'b', 'cin=0'

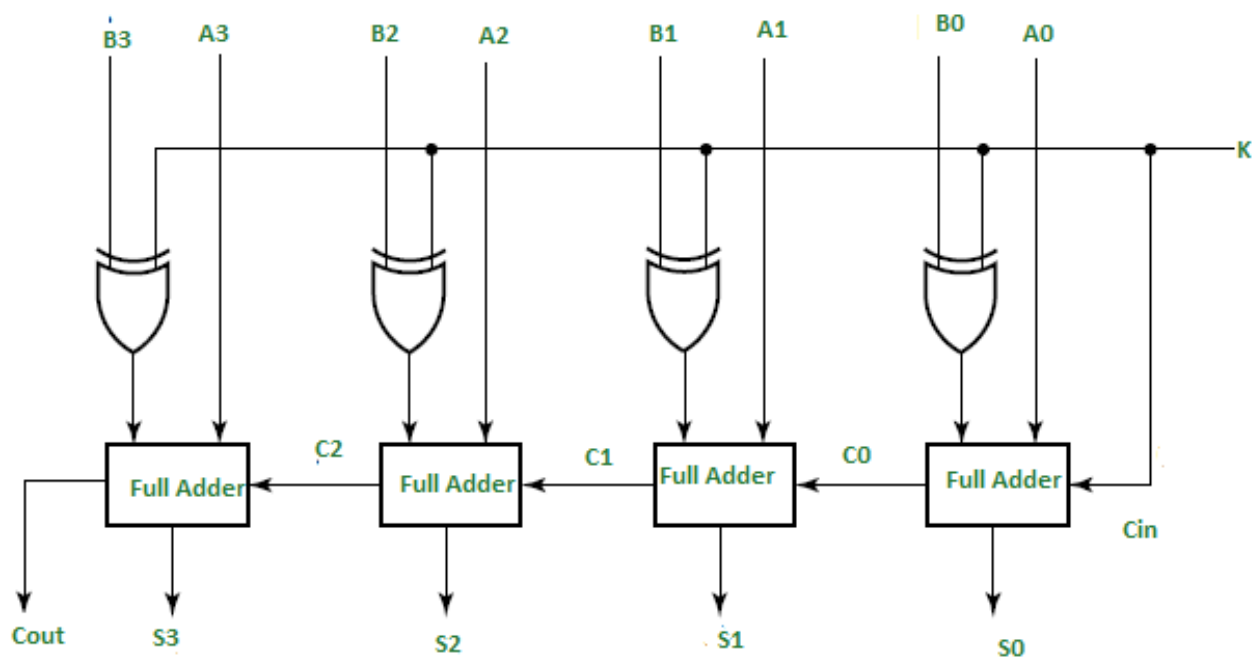
### **When cin = 1**

Input will be 'a', '1's complement of b', 'cin=1'

In this way we can use the 4 bit ripple carry adder for both the addition and subtraction of two 4 bit numbers known as a 4-bit ripple carry adder-subtractor, which is a single function for calculating both the addition and the subtraction.



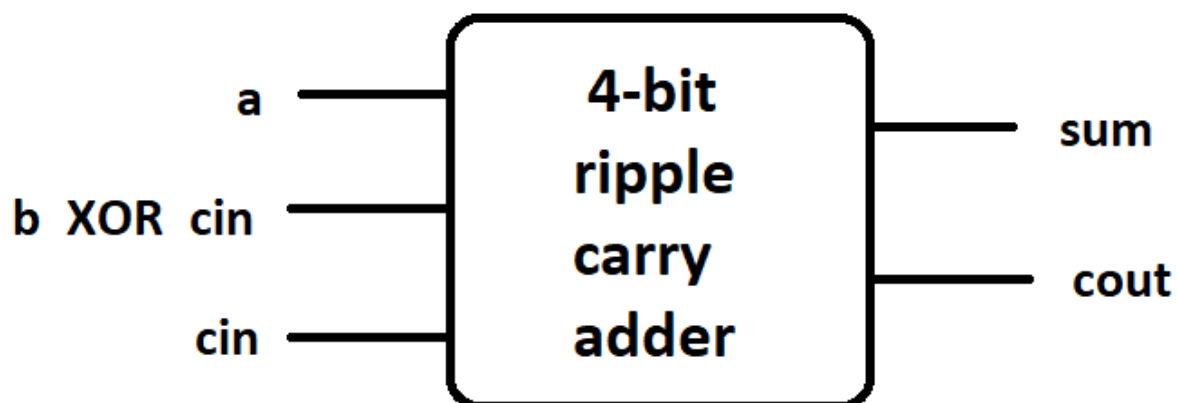The above diagram is using 4 1-bit full adder. But we have to use a 4-bit ripple adder which i am simply showing by a box below. The internal implementation is clearly shown in the above diagram.



### Analysis of the two cases possible:

#### **Case-1:**

$cin = 0$  So  $b \text{ XOR } cin = b$  itself  
So final output =  $a + b$

#### **Case-2:**

$cin = 1$  So  $b \text{ XOR } cin = 1$ 's complement of  $b$   
And by adding 1's complement with the carry 1 present in  $cin$ , we finally get  
 $= a + 1$ 's complement of  $b + 1$   
 $= a + 2$ 's complement of  $b$   
 $= a - b$